
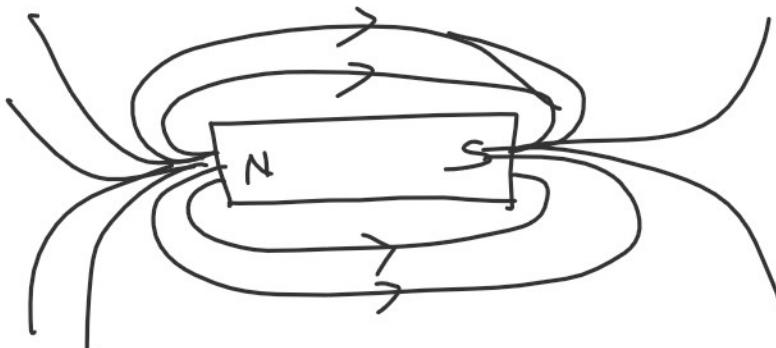


Inductor and Capacitor - Theoretical and Practical aspects

Faraday's Electromagnetic Induction Law

The induced electromotive force in any closed circuit is equal to the negative of the time rate of change of the magnetic flux enclosed by the circuit. "Faraday's Law, which states that the electromotive force around a closed path is equal to the negative of the time rate of change of magnetic flux enclosed by the path". Mathematically,
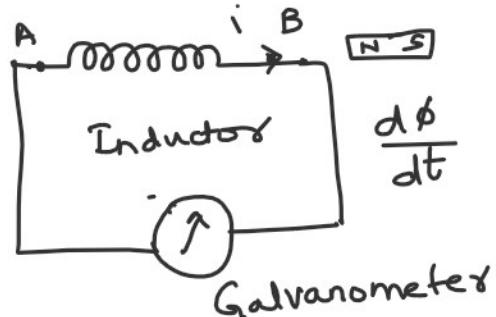
$$\epsilon = -N \frac{dB}{dt} = -NL \frac{dI}{dt}$$





Loop

Coil



Solenoid

Factors affecting Inductance of Inductor


No. of turns
 $L \propto N$

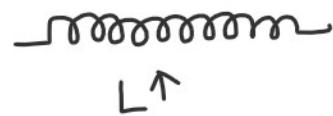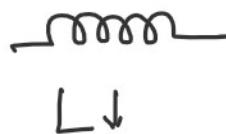



coil area

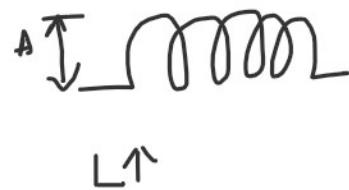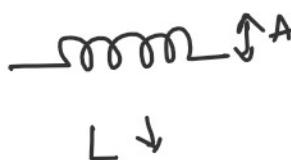

coil length

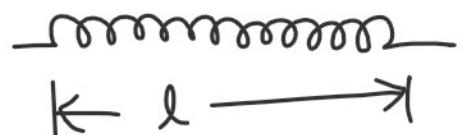

$L \propto \frac{1}{l}$

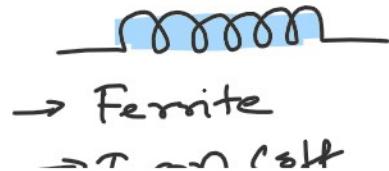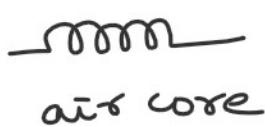

Core material

Core materials

$$L \propto \mu$$

air core
 $\mu = 1$

\rightarrow Ferrite
 \rightarrow Iron soft
 $\mu = 600$

$$L = \frac{\mu \cdot k N^2 \cdot A}{l}$$


$$X_L = \text{Inductive Reactance} = 2\pi f L$$

$$\underline{\text{Def:}} - 1 \text{ Henry} = \frac{1 \text{ Amp}}{1 \text{ sec}}$$

\uparrow 3.14
 \uparrow Inductance
 \uparrow freq: -50 Hz
 \uparrow freq: 50 Hz



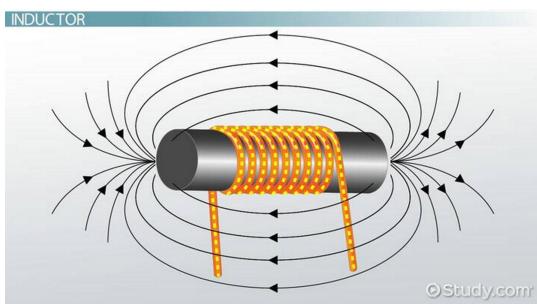
1. How to form an Inductor
2. Definition
3. Types of Inductors
4. Inductive reactance
5. Self inductance
6. V-I relationship
7. Energy





When the current thro' the coil
 is made to change $\ominus 1 \frac{\text{Amp}}{\text{sec}}$
 inducing a voltage of 1V.



Types of Inductors


Inductor Symbols

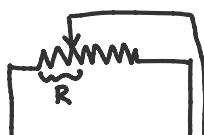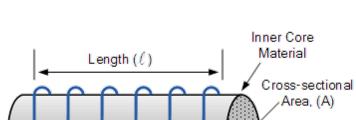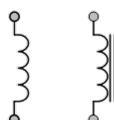


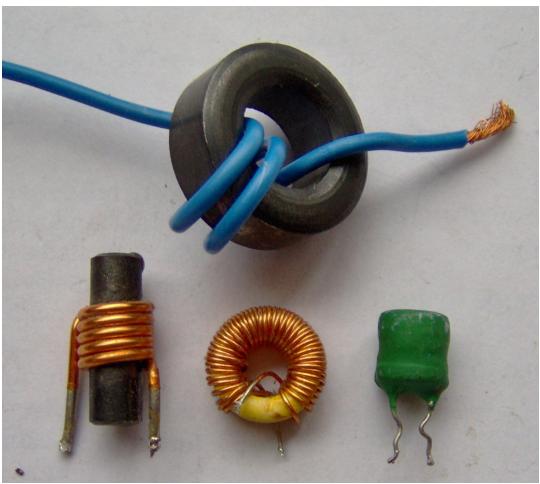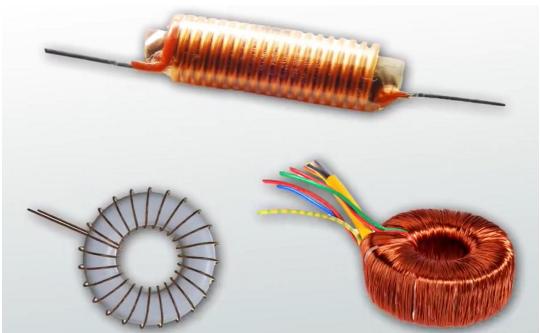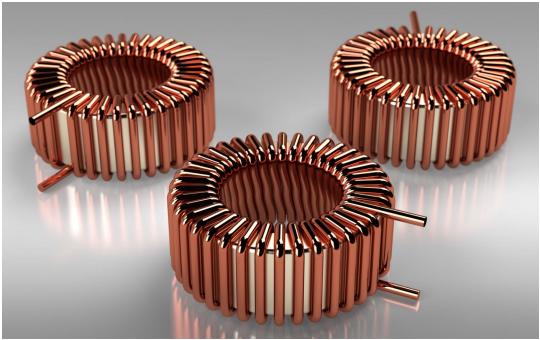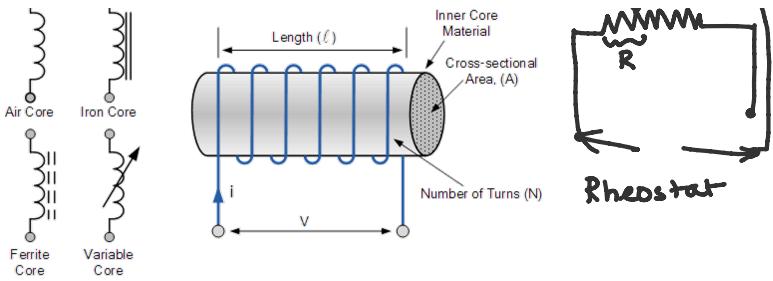

$$V_L = L \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{1}{L} \int V dt .$$

$$P = V \cdot I = V(t) i(t)$$

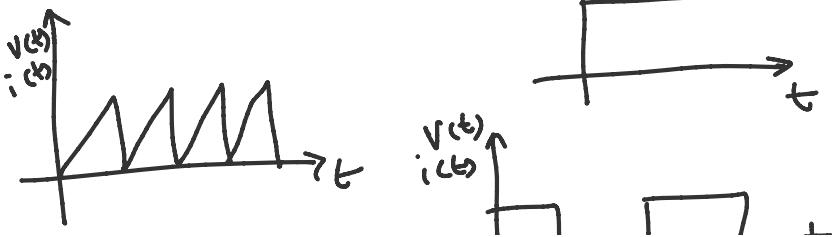


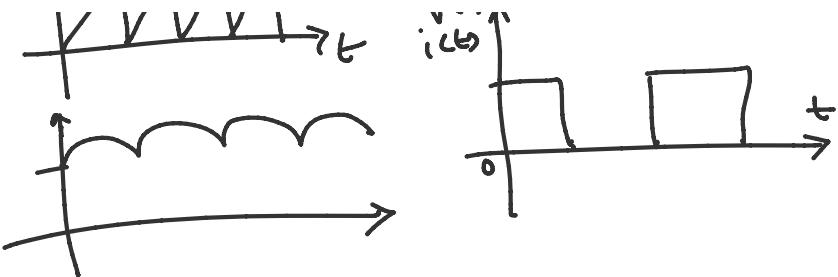

hmm



$$P = V i = L \frac{di}{dt} i = L i \frac{di}{dt}$$

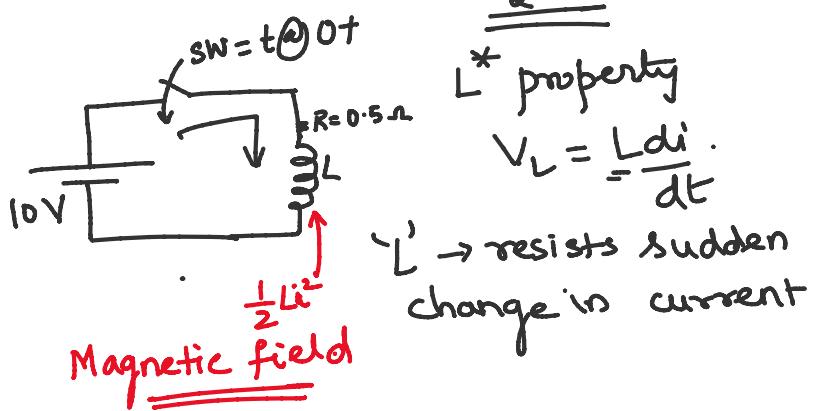
Energy by L stored / Dissipated $\gamma = \int_0^t \left(L i \frac{di}{dt} \right) dt = \frac{1}{2} L i^2$



At $t=0+$, $i=0$. 'L' acts like an open circuit

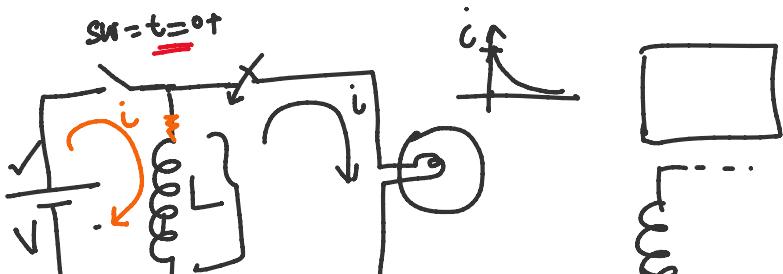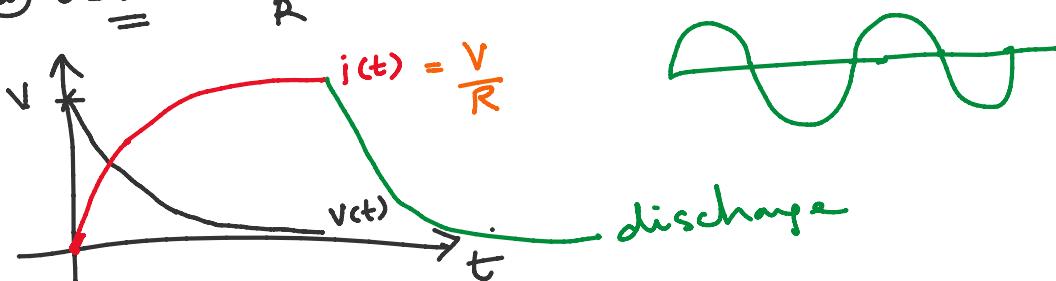At $t=\infty$, $i = \frac{V}{R}$. 'L' acts like a short circuit



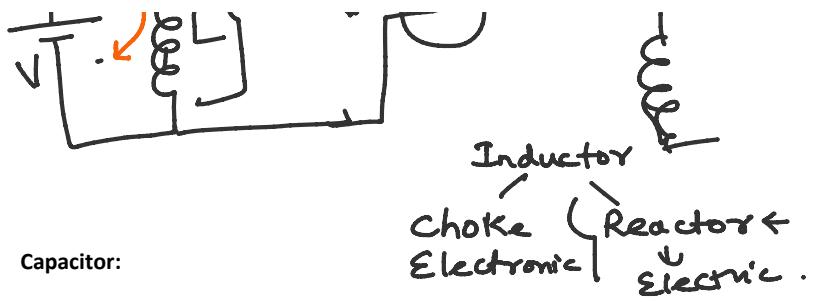

What is the Role of Capacitor in AC and DC Circuit?



10^{-3} mF, μ F, nF, pF
 $; 10^{-6}; 10^{-9}; 10^{-12}$



capacitor:

1 Farad

EV's


Super Capacitor
Ultra Capacitor

Practical Applications of Inductor

Tube light (Choke): The purpose of the choke is to provide a very high voltage initially between the filaments (across the two ends of the tube light). Again once the gas in the tube is ionized the choke provides a low voltage. A choke is a coil of wire.



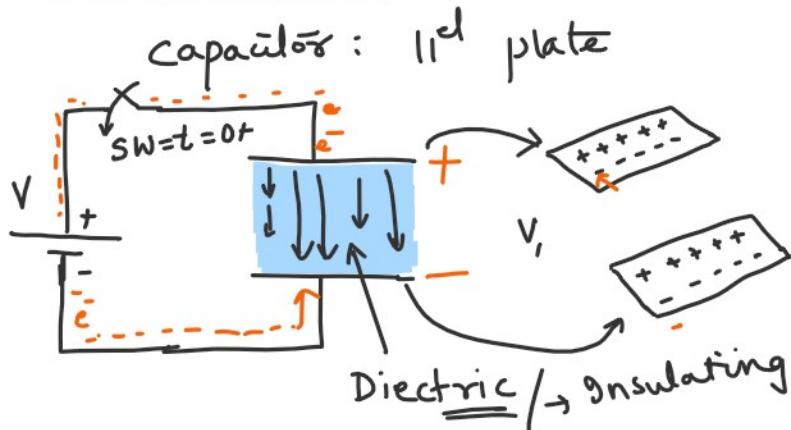Practical Applications of Capacitor: Ceiling Fan- for starting the Fan




Glass, ceramic, plastic film, mica, Air.
insulating paper, wax, oxide layer


10 C → A → 5 V

B ← 10 C → 2 V

$$C_A = \frac{q}{V} = \frac{10}{5} = 2 F$$

$$C_B = \frac{10}{2} = 5 F \checkmark$$

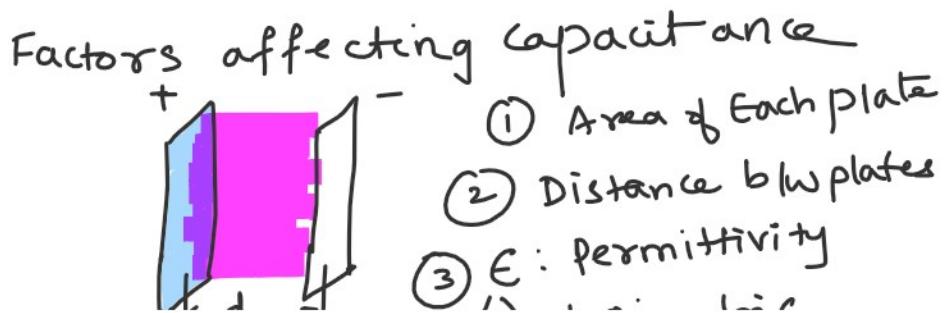

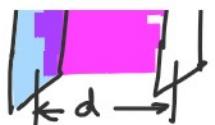

③ ϵ : Permittivity
of Dielectric material
 $\epsilon_0 \epsilon_r$

$$C = \frac{\epsilon A}{d}$$

$$\frac{Q}{V} = C$$

Farad

V-I


$$i = C \frac{dV}{dt}$$

$$v = L \frac{di}{dt}$$

Power : $P = v i = V C \frac{dV}{dt}$

Energy :- $\int_0^t P dt = \int_0^t C V \frac{dV}{dt} dt$

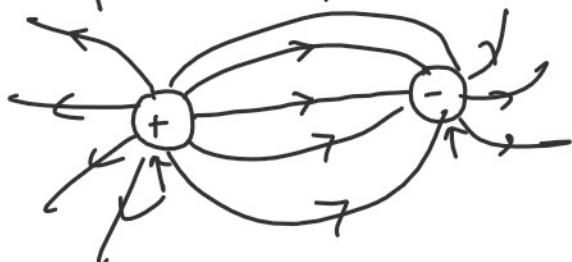
Energy stored or
dissipated in capacitor $\{ = \frac{1}{2} CV^2$



Capacitive Reactance :- $X_C = \frac{1}{2\pi f C}$

$f \rightarrow$ freq $\textcircled{a} \approx 10^4$

$C \rightarrow$ Capacitance in
Farad

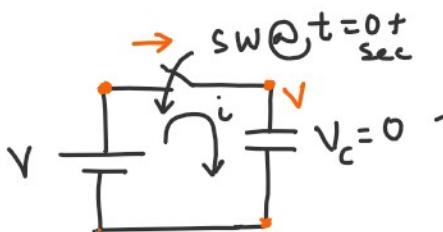

$$L \rightarrow \frac{di}{dt}$$

A capacitor Resists


$$C \rightarrow \frac{dV}{dt}$$

A capacitor Resists
fast change in voltage


$$C \rightarrow \frac{du}{dt}$$

@) $t = 0^+$; Capacitor acts like S.C

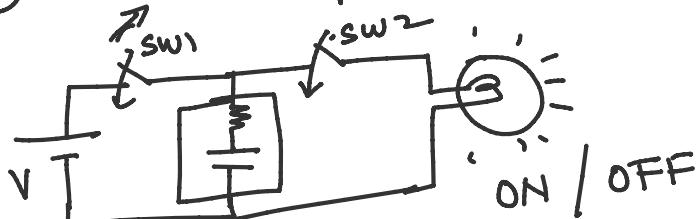@) $t \rightarrow \infty$; Capacitor " " " O.C



R-L Response due to DC excitation

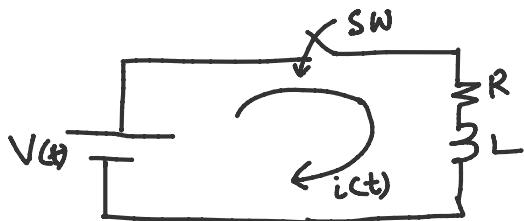

$$\underbrace{V - iR}_{u} - L \frac{di}{dt} = 0$$

$$u = L \frac{di}{dt}$$

Integrate on both sides

$$\int_0^t \frac{dt}{L} = \int_0^i \frac{di}{u}$$

$$\frac{t}{L} = \int_0^i -\frac{du}{R \cdot u} \Rightarrow \frac{-1}{R} \left[\log_e u \right]_0^i$$

- ✓ ① differentiation
- ✓ ② Laplace Transform

$$u = V - iR$$

$$\frac{du}{di} = -R$$

$$di = -\frac{du}{R}$$

$$\frac{t}{L} = \int_0^t \frac{1}{R \cdot u} \cdot R I \, du$$

$$\frac{t}{L} = -\frac{1}{R} \left[\log_e \frac{V - iR}{V} \right]_0^t$$

$$= -\frac{1}{R} \left[\ln(V - iR) - \ln V \right]$$

$$= -\frac{1}{R} \left[\ln \left[\frac{V - iR}{V} \right] \right]$$

antilog

$$\text{antilog} \left[\log_e \frac{V - iR}{V} \right] = -\frac{Rt}{L}$$

$$-\frac{Rt}{L}$$



$$\frac{V - iR}{V} = e^{-\frac{Rt}{L}}$$

$$1 - \frac{iR}{V} = e^{-\frac{Rt}{L}}$$

✓

$$i(t) = \frac{V}{R} \left[1 - e^{-\frac{Rt}{L}} \right]$$
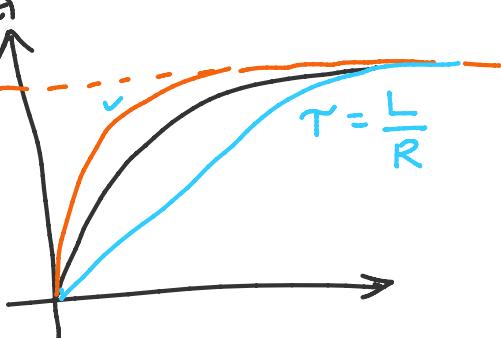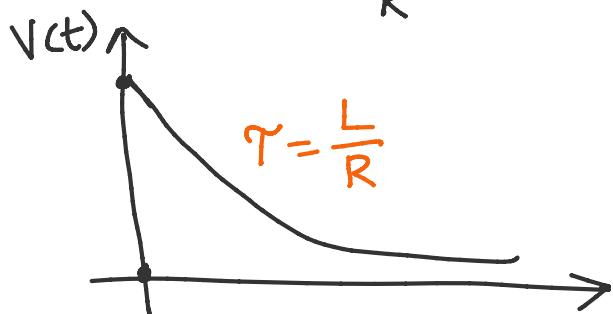
$$i(t) = \frac{V}{R} - \frac{V}{R} e^{-\frac{Rt}{L}}$$



✓

$$V_R = i \cdot R = V \left[1 - e^{-\frac{Rt}{L}} \right]$$

$$-Rt \rightarrow$$

$$\checkmark V_R = L \cdot K = V [1 - e^{-\frac{Rt}{L}}]$$

$$\checkmark V_L = L \frac{di}{dt} = \frac{V}{R} \cdot K \left[\frac{R}{L} \cdot e^{-\frac{Rt}{L}} \right]$$


$$V_L = V e^{-\frac{Rt}{L}}$$

$$\checkmark P_R = V_R \cdot i = V \left[1 - e^{-\frac{Rt}{L}} \right] \frac{V}{R} \left[1 - e^{-\frac{Rt}{L}} \right]$$

$$= \frac{V^2}{R} \left[1 + e^{-\frac{2Rt}{L}} - 2e^{-\frac{Rt}{L}} \right]$$


$$\checkmark P_L = V_L \cdot i = \frac{V \cdot V}{R} e^{-\frac{Rt}{L}} \left[1 - e^{-\frac{Rt}{L}} \right]$$
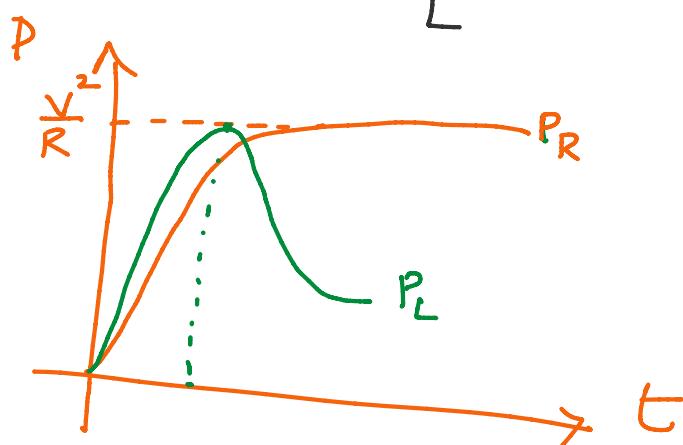
$$= \frac{V^2}{R} \left[e^{-\frac{Rt}{L}} - e^{-\frac{2Rt}{L}} \right]$$




② Response due to DC excitation in an R-C circuit.

$$C = \frac{q}{V_c}$$

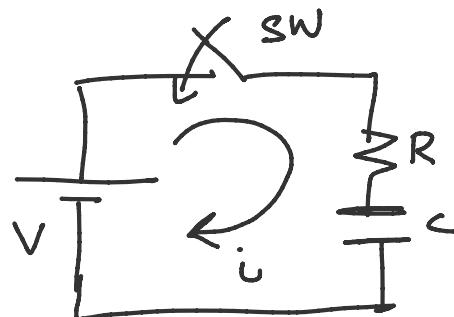

$$-\overline{V_c}$$

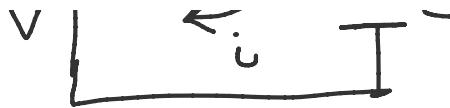

$$\dot{i} = \frac{dq_v}{dt}$$

$$V = iR + \frac{1}{C} \int i dt$$

$$V = \frac{dq_v}{dt} R + \frac{q_v}{C}$$

$$\left(V - \frac{q_v}{C} \right) = \frac{d q_v}{dt} \cdot R$$

$$\int_0^t \frac{dt}{R} = \int_0^q_v \frac{d q_v}{\left(V - \frac{q_v}{C} \right)}$$

$$V - \frac{q_v}{C} = u$$

$$\frac{du}{dq_v} = -\frac{1}{C}$$

$$dq_v = -du \cdot C$$

$$\frac{t}{R} = -c \left[\ln \left(V - \frac{q_v}{C} \right) \right]_0$$

$$\frac{-t}{RC} = \left[\ln \left(V - \frac{q_v}{C} \right) - \ln V \right]$$

$$\frac{-t}{RC} = \ln \left[\frac{V - q_v/C}{V} \right]$$

antilog

$$-t/RC$$

$$\frac{V - q_v/C}{V} = e^{-t/RC}$$

$$1 - \frac{q_v}{V} = e^{-t/RC}$$

$$\frac{q}{V_C} = \left[1 - e^{-t/RC} \right] \Rightarrow \frac{q}{C} = V \left[1 - e^{-t/RC} \right]$$




$$V_C = V \left[1 - e^{-t/RC} \right]$$

$$i(t) = C \frac{dV_C}{dt}$$

$$= C V \left[-e^{-t/RC} \left(\frac{-1}{RC} \right) \right]$$

\checkmark
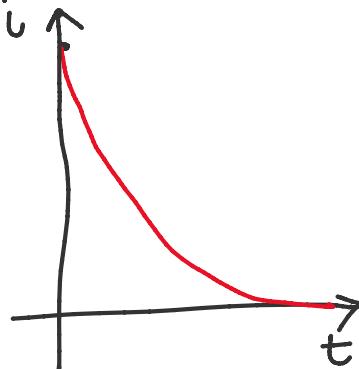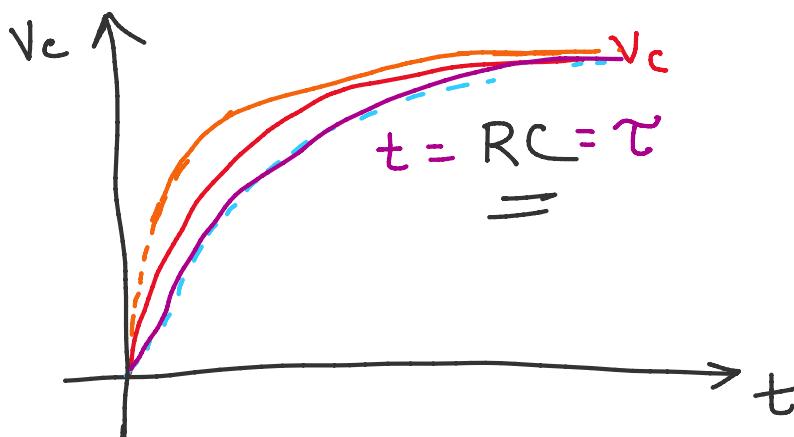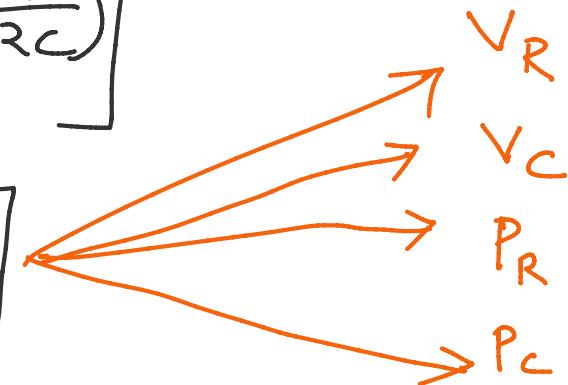
$$i(t) = \frac{V}{R} \left[e^{-t/RC} \right]$$



$$V_R = i R = \frac{V}{R} e^{-t/RC} \cdot R = V e^{-t/RC}$$

$$V_C = V \left[1 - e^{-t/RC} \right]$$

$$P_R = V_R i = V e^{-t/RC} \cdot \frac{V}{R} e^{-t/RC} = \frac{V^2}{R} e^{-2t/RC}$$

$$V_R = V_{R^C} = V e^{-\frac{t}{RC}} = \frac{V}{R} e^{-\frac{t}{RC}}$$

$$\begin{aligned} P_C &= V_C \cdot i = V \left[1 - e^{-\frac{t}{RC}} \right] \frac{V}{R} \left[e^{-\frac{t}{RC}} \right] \\ &= \frac{V^2}{R} \left[e^{-\frac{t}{RC}} - e^{-\frac{2t}{RC}} \right] \end{aligned}$$

$$t=0 ; P_C=0$$

$$t=\infty ; P_C=0$$

