

## FAST MULTIPLIERS

- Combinational array multiplier
- Sequential circuit binary multiplier
- Booth method
- ~~- Bit pair recoding~~

## Carry Save addition



- Unsigned number multiplication

$$\underline{n=4} \quad \left\{ \begin{array}{l} \text{Multiplicand - } M \\ \text{Multiplier - } Q \end{array} \right.$$

2n bits      Product -  $P = M \times Q$

$$\begin{array}{ccccccc}
 m_3 & m_2 & m_1 & m_0 & \times q_3 & q_2 & q_1 & q_0 \\
 \hline
 & & & & & & & \\
 m_3q_0 & m_2q_0 & m_1q_0 & m_0q_0 & \longrightarrow PP_0 \rightarrow A \\
 m_3q_1 & m_2q_1 & m_1q_1 & m_0q_1 & \longrightarrow PP_1 \rightarrow B \\
 m_3q_2 & m_2q_2 & m_1q_2 & m_0q_2 & \longrightarrow PP_2 \rightarrow C \\
 m_3q_3 & m_2q_3 & m_1q_3 & m_0q_3 & \longrightarrow PP_3 \rightarrow D \\
 \hline
 P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}$$

Basic cell

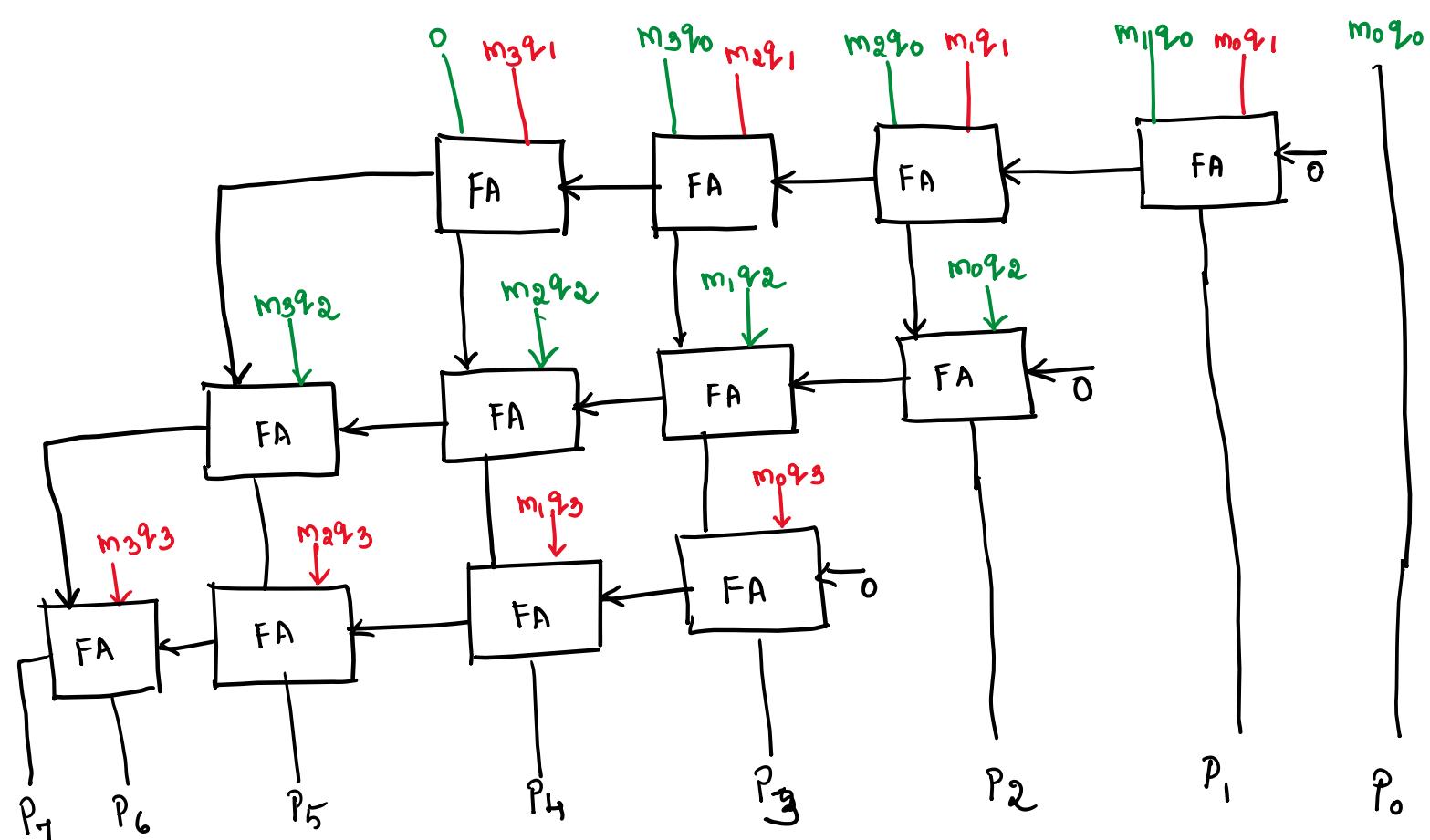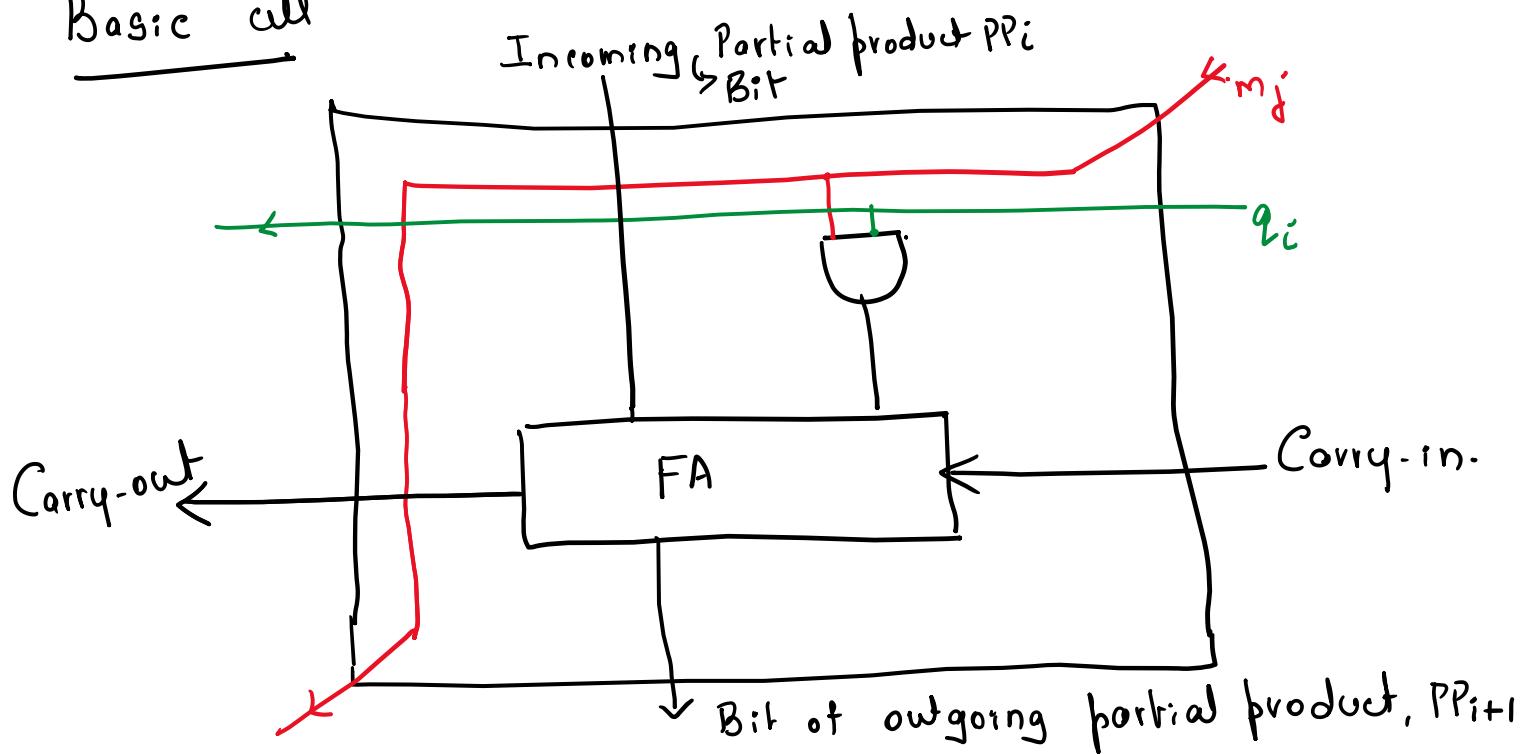

Ripple - carry array

Give the carry for next level.

Carry Give Addition

$$\begin{array}{r}
 X \quad 00110 \\
 Y \quad 00011 \\
 \hline
 \text{Normal binary addition} \quad 1 \quad 0 \\
 \begin{array}{r}
 X \\
 + Y \\
 \hline
 Z
 \end{array}
 \quad \begin{array}{r}
 0 \quad 0 \quad | \quad 1 \quad 1 \quad 0 \\
 0 \quad 0 \quad 0 \quad | \quad 1 \quad 1 \\
 \hline
 0 \quad | \quad 0 \quad 0 \quad 1
 \end{array}
 \end{array}$$


CSA

$$\begin{array}{r}
 S \rightarrow \quad 0 \quad 0 \quad 1 \quad 1 \quad 0 \\
 0 \quad 0 \quad 0 \quad 1 \quad 1 \\
 \hline
 0 \quad 0 \quad | \quad 0 \quad 1
 \end{array}$$

$$C \rightarrow \quad 0 \quad 0 \quad 0 \quad 1 \quad 0$$

$$\begin{array}{r}
 S \quad 0 \quad 0 \quad 1 \quad 0 \quad 1 \\
 0 \quad 0 \quad 0 \quad 1 \quad 0 \\
 \hline
 0 \quad | \quad 0 \quad 0 \quad 1
 \end{array}$$

Array multiplier

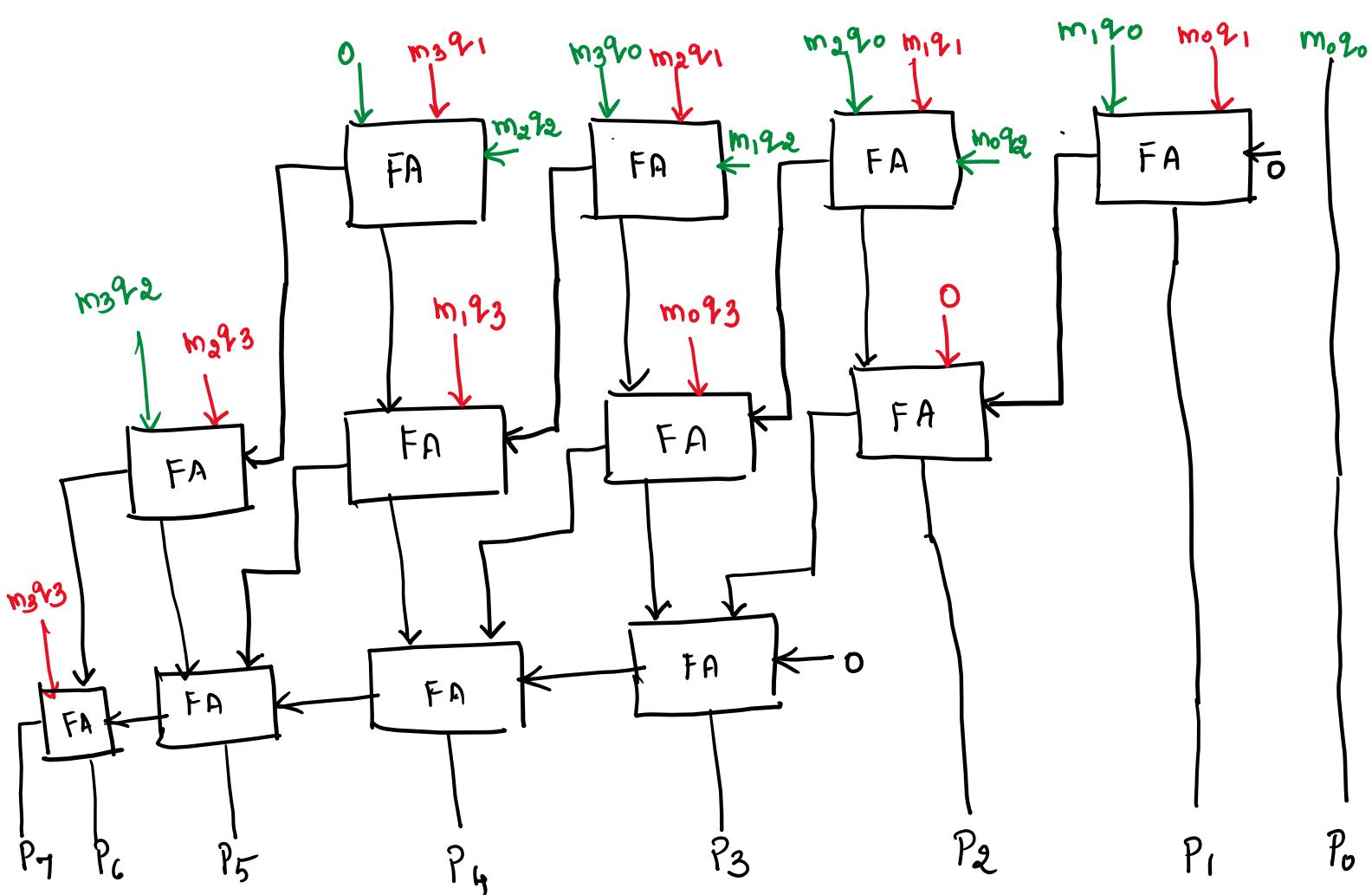

I Row:  $PP_0, PP_1, PP_2$

Sum Vector —  $S_1$

Carry Vector —  $C_2$

II Row:  $PP_3, S_1, C_2$

Sum Vector and a Carry Vector.

$S_2$


$C_2$

III Row

$S_2$   
 $C_2$

RCA

P

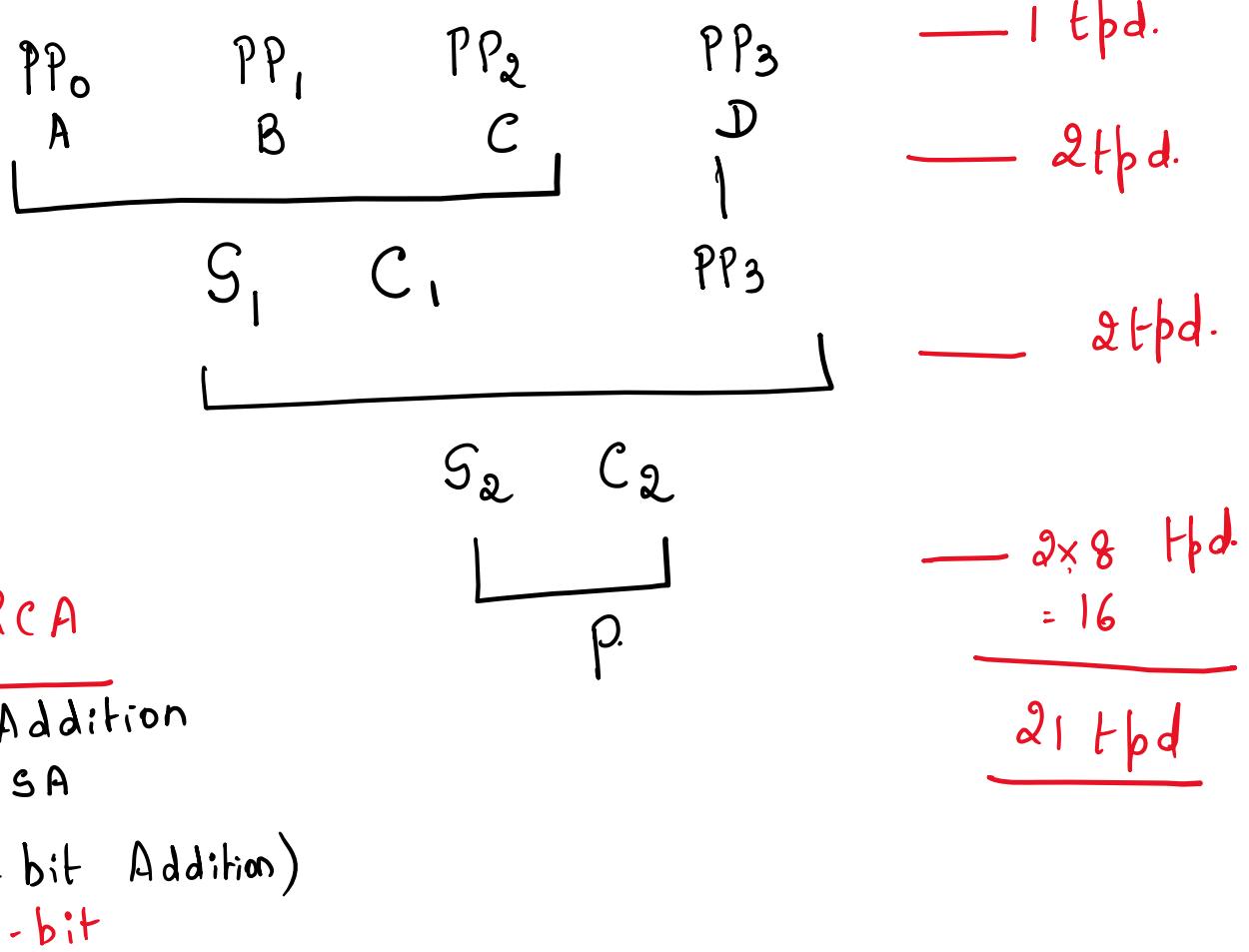

Operands n=4 bits : Unsigned numbers

① Combinational array multiplier:  $6(n-1) - 1$

$$= 6(4-1) - 1$$

$$= 18 - 1$$

$$= \underline{\underline{17 \text{ tpd}}}$$

② CSA - array : RCA

Partial product bit generation = 1 tpd

I CSA = 2 tpd

II CSA = 2 tpd

Last level RCA - normal addition. =  $2 \times 8 = 16 \text{ tpd}$   
 $(8\text{-bit})$

$$\underline{\underline{21 \text{ tpd}}}$$

### ③ CSA array - CLA in last Inv.

Partial product bit generation = 1 tpd.

$$\text{I} \quad \text{CSA} \quad = 2 \text{ tpd.}$$

$$\text{II} \quad \text{CSA} \quad = 2 \text{ tpd.}$$

8-bit CLA? Built using  
Four bit CLA

$$K \quad \quad \quad l \quad \quad \quad = 2 \cdot \frac{K}{l} + 2 \\ = 2 \times \frac{8}{4} + 2$$

$$= 6 \text{ tpd.}$$

$$\text{Total} = \underline{\underline{11 \text{ tpd.}}}$$

More significant reduction in delay can be achieved  
when having large number of summands.

↳ Large n

$$M = 45$$

6-bit representation

$$Q = 63$$


6 PPs  
6 Summands


$$\underline{P = 2835} \quad \rightarrow 12 \text{ bits}$$

1 0 1 1 0 1 M(45)

1 1 1 1 1 1 A(63)

1	0	1	1	0	1	$\overline{PP_0}$	A
1	0	1	1	0	1	$\overline{PP_1}$	B
1	0	1	1	0	1	$\overline{PP_2}$	C
1	0	1	1	0	1	$\overline{PP_3}$	D
1	0	1	1	0	1	$\overline{PP_4}$	E
1	0	1	1	0	1	$\overline{PP_5}$	F
1	0	1	1	0	0	0	1
1	0	1	1	0	0	0	1

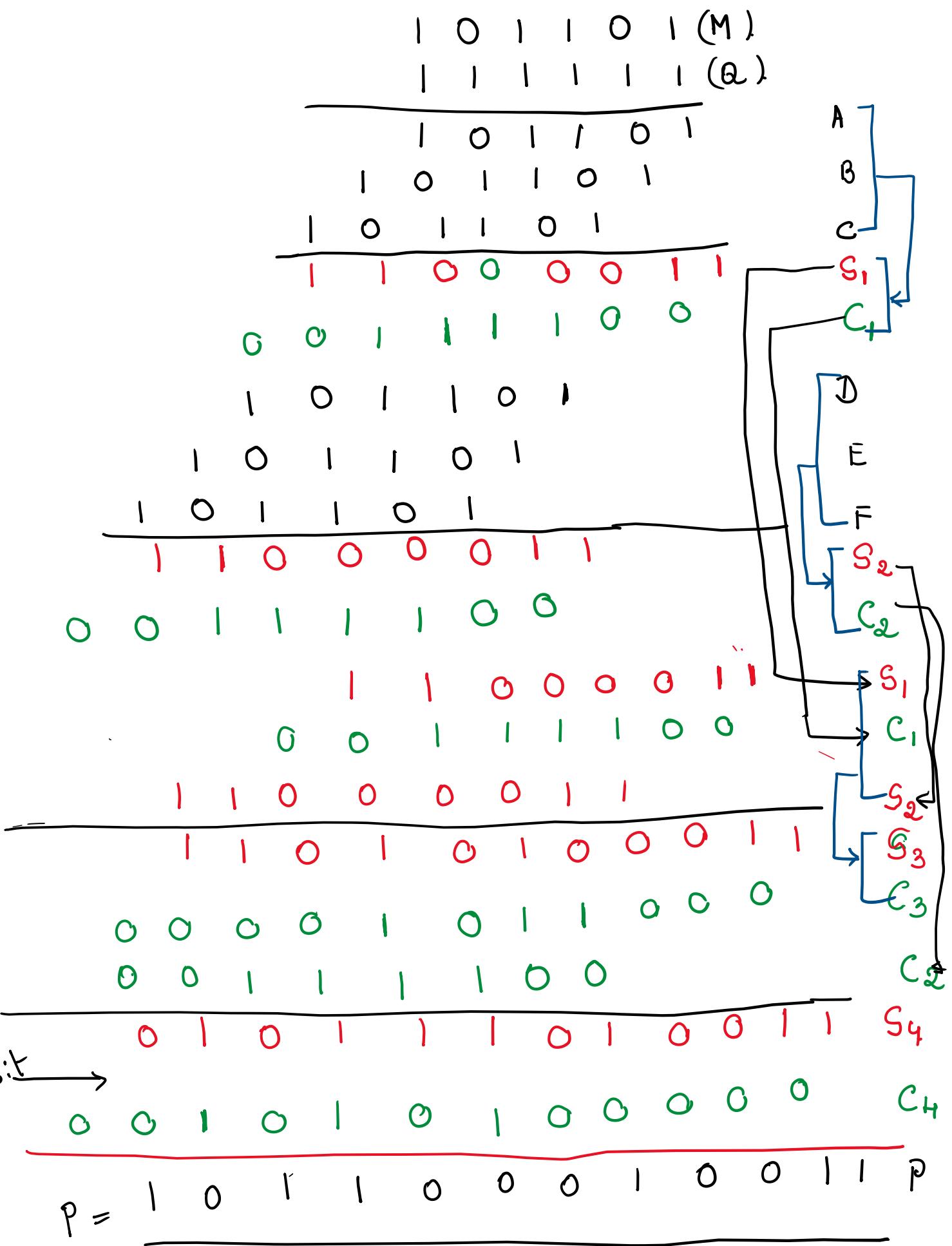

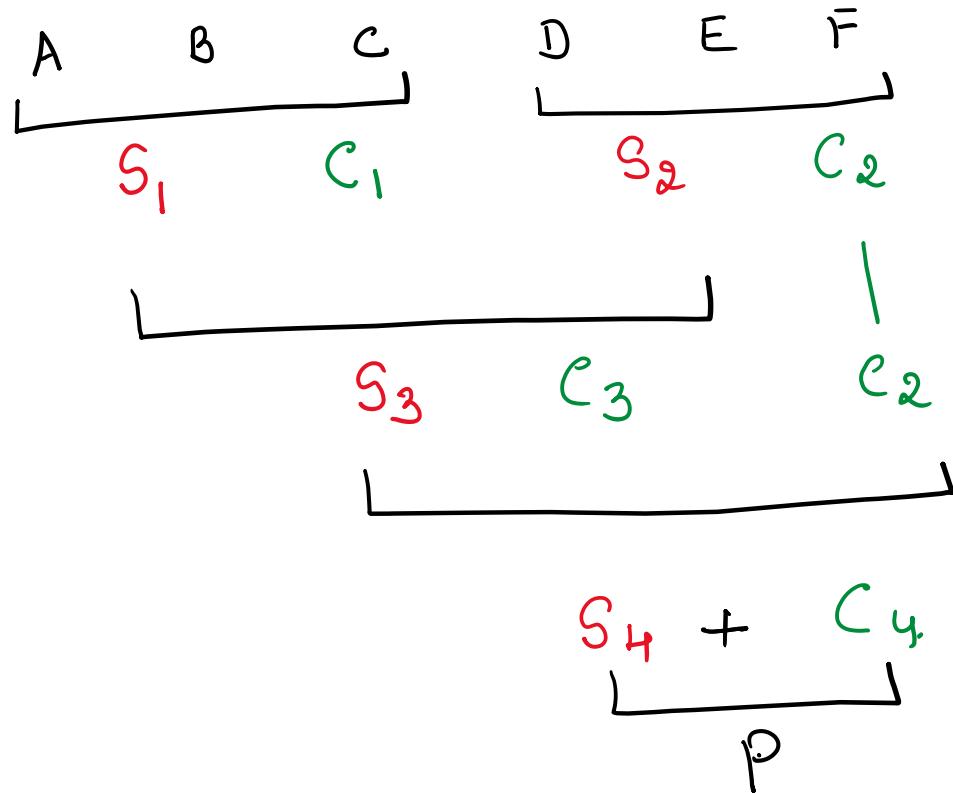

### 6-bit multiplication

$$\begin{aligned}
 \textcircled{1} \text{ Combinational array multiplier: } & 6(n-1)-1 \\
 & = 6(6-1)-1 \\
 & = \underline{29 \text{ f.p.d}}
 \end{aligned}$$

\textcircled{2} CSA Using RCA (12-bit)

Partial product bit generation = 1 f.p.d.

$$\text{I CSA} = 2 \text{ f.p.d.}$$

$$\text{CSA - II} = 2 \text{ f.p.d.}$$

$$\text{CSA - III} = \underline{\underline{2 \text{ f.p.d.}}}$$

$$12\text{-bit - } \text{RCA} = \underline{\underline{2 \times 12 = 24 \text{ bit}}}$$



$$\text{Total} = 311 \text{ f.p.d.}$$

③ CSA - 12 bit addition CLA - 4-bit CLAS

$$\text{Delay in last layer} = 2 \cdot \frac{12}{4} + 2 \\ = 8 \text{ tpd.}$$

$$\text{Total} = 15 \text{ tpd}$$

8-bit Multiplication

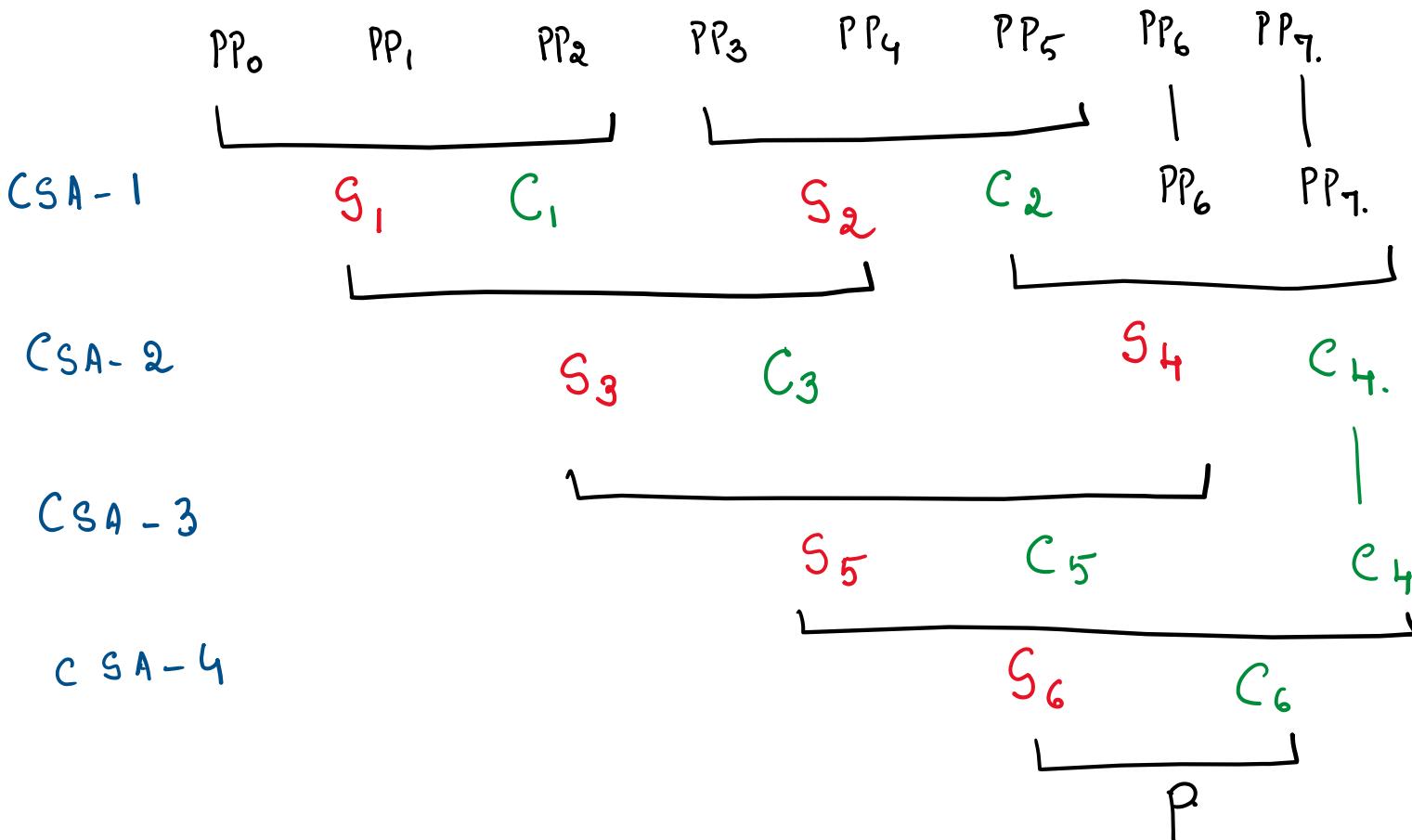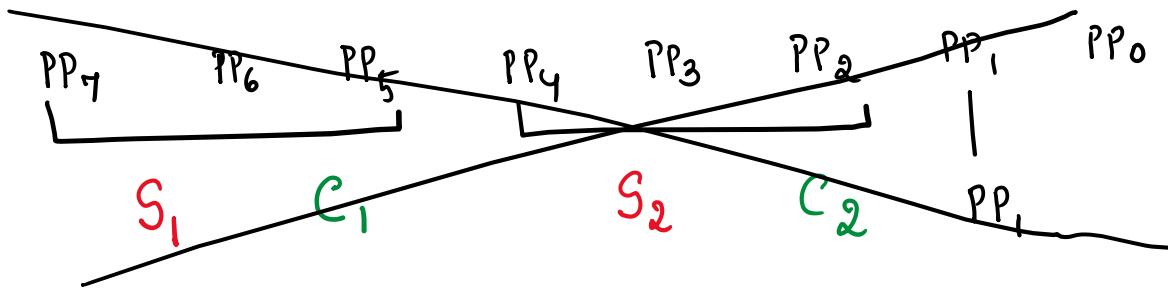

Partial product bit generation : 1 tpd.

Number of CSA levels : 4.

Delay in 4 levels of CSA =  $4 \times 2 = 8 \text{ tpd}$ .

16-bit adder (CLA) - 4-bit CLAs :

$$2 \times \frac{4}{4} + 2 = 10 \text{ tpd.}$$

$$\text{Total} = 1 + 8 + 10$$

$$= \underline{19 \text{ tpd}}$$

### Generalized delay computation

PP bit generation = 1 tpd.

Delay through 'm' CSA levels =  $2 \times m \text{ tpd}$ .

2n bit CLA built using 1 bit CLAs =  $2 \cdot \frac{2n}{1} + 2$

$$\boxed{\text{Total} = 1 + 2m + 2 \cdot \frac{2n}{1} + 2}$$

### How to decide m?

16-bit operands - 16 bps

Total.	Level	Grouped	Pending
16	I	15	1
11	II	9	2
8	III	6	2
6	IV	6	0
4	V	3	1
3	VI	1	
<u><u>2</u></u>			

$$\underline{m = 6}$$

K submands

$$m = 1 \cdot 7 \log_2 K - 1 \cdot 7$$

$$K = 16.$$

$$m = 1 \cdot 7 \log_2 16 - 1 \cdot 7$$

$$= 1 \cdot 7 \log_2 2^4 - 1 \cdot 7$$

$$= 1 \cdot 7 \times 4 - 1 \cdot 7$$

$$= 5 \cdot 1 \approx 6$$

$$K = 8.$$

$$m = 1 \cdot 7 \log_2 2^3 - 1 \cdot 7$$

$$= 1 \cdot 7 \times 3 - 1 \cdot 7$$

$$= 3 \cdot 4$$

$$\approx \underline{\underline{4}}$$