
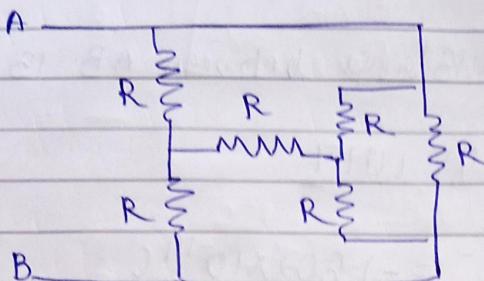


BES Mid Sem Exam
SECTION A

Q1)

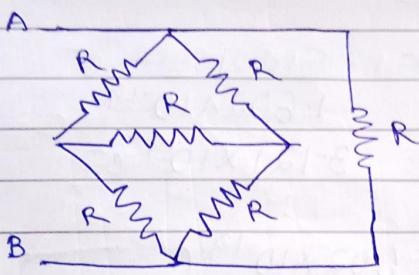

Can be simplified as




Using Delta to Star transformation

$$\begin{array}{c} \Delta: \\ \text{RA} \quad \text{RB} \quad \text{RC} \\ | \quad | \quad | \\ \text{RAB} \quad \text{RBC} \quad \text{RCA} \\ | \quad | \quad | \\ \text{RA} \end{array} \Rightarrow \begin{array}{c} \text{RA} \\ | \\ \text{RB} \quad \text{RC} \\ | \quad | \\ \text{RB} \quad \text{RC} \end{array}$$


$$\therefore \text{RA} = \frac{\text{RAB} \cdot \text{RCA}}{\text{RAB} + \text{RCA} + \text{RBC}} = \frac{\text{R}^2}{3\text{R}} = \frac{\text{R}}{3}$$

$$\text{RB} = \frac{\text{RAB} \cdot \text{RBC}}{\text{RAB} + \text{RBC} + \text{RCA}} = \frac{\text{R}^2}{3\text{R}} = \frac{\text{R}}{3}$$
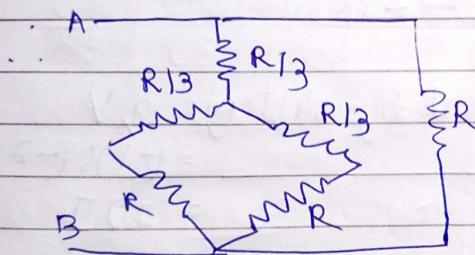
$$\text{RC} = \frac{\text{RCA} \cdot \text{RBL}}{\text{RCA} + \text{RBL} + \text{RAB}} = \frac{\text{R}^2}{3\text{R}} = \frac{\text{R}}{3}$$




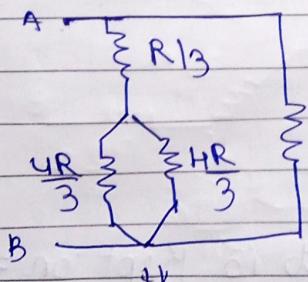
$$\therefore \frac{R}{3} \text{ and } R \text{ are in series} \quad \text{Req} = \frac{R + R}{3} = \frac{4R}{3}$$



$$\therefore \frac{4R}{3} \text{ both are in II}$$
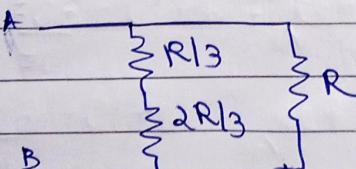
$$\text{Req}_2 = \frac{1}{\frac{4R}{3} + \frac{3}{4R}} = \frac{4R - 2R}{6} = \frac{2R}{6} = \frac{R}{3}$$



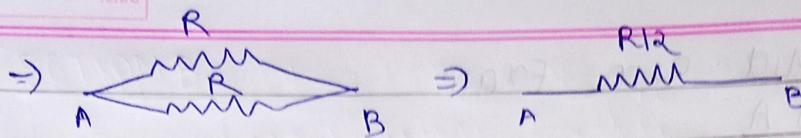

\therefore Equivalent resistance between AB is $R = \frac{R}{2} + \frac{R}{2}$

ROLL NO is 20CGSE1017

Ans 2) Charge on FE $1e^- = -1.602 \times 10^{-19} C$
 No. of e^- in $1C = \frac{1}{1.602 \times 10^{-19}} e^-$

\therefore No. of e^- in $-5C = \frac{5 \times 1}{1.602 \times 10^{-19}} e^-$
 $= 3.121 \times 10^{19} e^-$

Ans 3) Charge on $1e^- = -1.602 \times 10^{-19} C$
 charge on $6.28 \times 10^{18} e^- = +6.28 \times 10^{18} \times -1.602 \times 10^{-19}$
 $\approx -1C$

Energy used or supplied by battery = qV
 $= (-1)(-20V)$
 $= 20 J$


4) ~~The conductor~~

Ans 4) Copper

Ans 5) 0K or $-273.15^\circ C$

Ans 6) Time for which the bulb is kept on = 12 hours
 $= 12 \times 60 \times 60$
 $= 43,200 s$
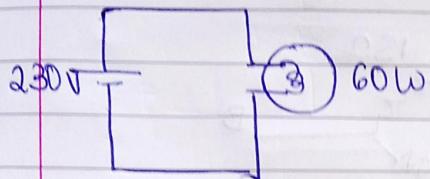
$$\begin{aligned}
 \text{Energy dissipated} &= \int P dt \\
 &= Pt \quad (\text{For constant power}) \\
 &= 60 \times 43,200 \\
 &= 2,592,000 \text{ J or } 60 \times 12 \text{ Whr} \\
 &\text{or } 720 \text{ Whr } 720 \text{ Whr}
 \end{aligned}$$




$$\begin{aligned}
 \therefore P &= VI \\
 &= V \left(\frac{V}{R} \right) \\
 &P = \frac{V^2}{R}
 \end{aligned}$$

$$V = iR$$

$$60 = \frac{(230)^2}{R} \Rightarrow R = \frac{(230)^2}{60} = 881.66 \Omega$$

Ans)

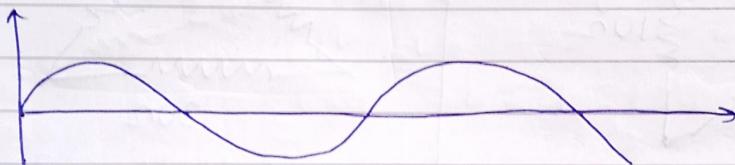

$$F = \omega = 2\pi f$$

80 Hz means 80 cycles in 1 sec

$$\therefore \text{No of cycles in 1 sec} = \frac{1}{80}$$

80 Hz mean 80 cycles in 1 sec

Let the time duration of each cycle be T

$$\therefore 80T = 1 \text{ s}$$


$$T = \frac{1}{80} \text{ s}$$

$$T = \frac{1000 \text{ ms}}{80}$$


$$= 12.5 \text{ ms}$$

SECTION B


Ans 8)

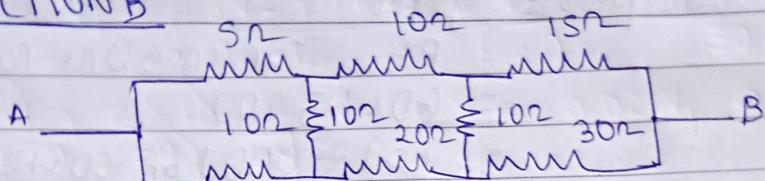

S can be written as

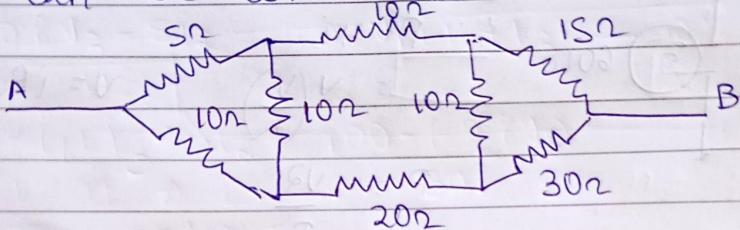


Using delta to star transformations

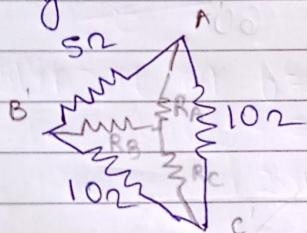

$$RA = \frac{5 \times 10}{5+10+10} = \frac{50}{25} = 2\Omega$$

$$RB = \frac{5 \times 10}{5+10+10} = \frac{50}{25} = 2\Omega$$
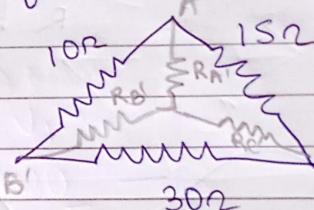
$$RC = \frac{100}{5+10+10} = \frac{100}{25} = 4\Omega$$




$$RA' = \frac{10 \times 15}{10+15+30} = \frac{150}{55} = 3\Omega$$

$$RB' = \frac{10 \times 30}{10+15+30} = \frac{300}{55} = 6\Omega$$


$$RC' = \frac{30 \times 15}{10+15+30} = \frac{450}{55} = 9\Omega$$

∴ The equivalent ckt is

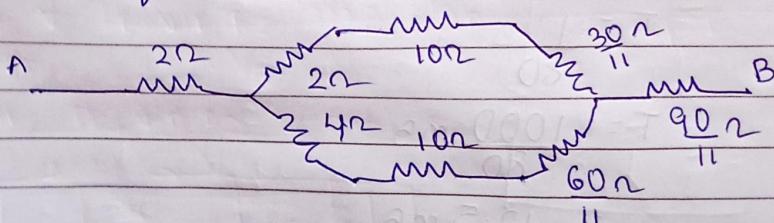


$$\text{For series resistors } R_{eq1} = \frac{2+10+30}{11} = \frac{42}{11} \Omega$$
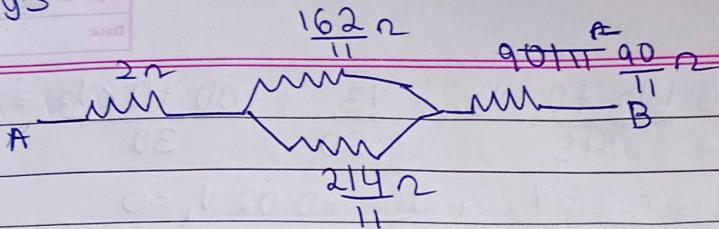
$$\dots \quad \text{“} \quad R_{eq2} = \frac{4+10+60}{11} = \frac{74}{11} \Omega$$



For Parallel resistors $R_{AB} = \frac{1}{\frac{1}{162} + \frac{1}{214}}$

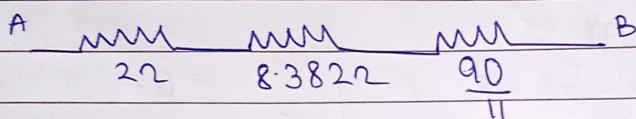
$$= \frac{1}{\frac{162 \times 214}{162 + 214}} = \frac{1}{\frac{162 \times 214}{376}} = 8.382 \Omega$$



\therefore Resistance b/w A and B = $2 + 8.382 + \frac{90}{11}$ (for sum)

$$= 18.564 \Omega$$

ANSW)

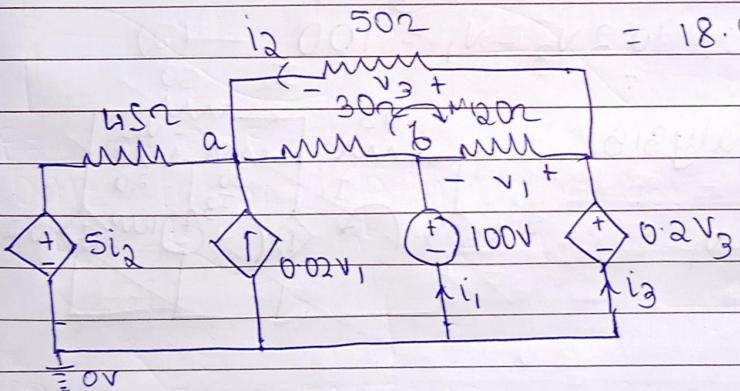

a) Nodal Analysis at a

$$\text{Potential at } a = +0.2v_3 - v_3 \\ = -0.8v_3$$

b) Nodal analysis at a

$$0.02v_1 + \frac{5i_2 - (-0.8v_3)}{4.5} + i_2 + \frac{100 - (-0.8v_3)}{30} = 0$$

$$\text{where } v_3 = \frac{i_2}{50}$$

$$0.1v_3 = 5i_2$$

$$0.02V_1 - \frac{0.1V_3 + 0.8V_3}{45} + \frac{V_3}{50} + \frac{100 + 0.8V_3}{30} = 0$$

$$\left(\frac{1}{50} + \frac{0.8}{30} + \frac{0.9}{45}\right)V_3 + \frac{10}{3} + 0.02V_1 = 0$$

$$\frac{V_3}{15} + \frac{V_1}{50} + \frac{10}{3} = 0 \quad \text{--- (1)}$$

$$-\frac{0.8V_3}{45} - i_2 = 0.02V_1 + i_1 + i_3 \quad \text{--- (2)}$$

$$i_1 + i_3 = i_2 + \frac{100 - 0.8V_3}{30} \quad \text{--- (3)}$$


From (1) and (2)

$$-\frac{0.9V_3}{45} =$$

Potential at b = +100

$$= +0.2V_3 - V_1$$
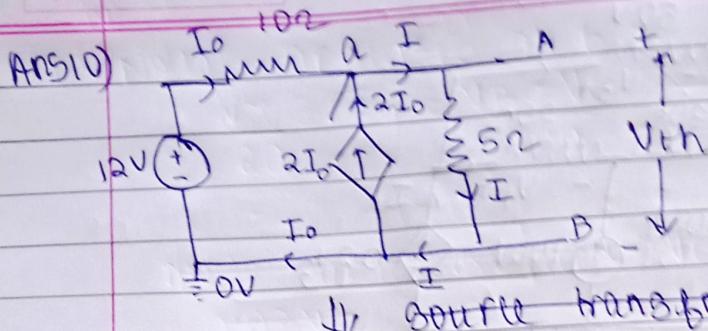
$$0.2V_3 - V_1 = 100 \quad \text{--- (2)}$$



KCL at $\Delta \Delta$

$$I_0 + 2I_0 = I$$

$$3I_0 = I$$

KVL in the bigger loop mesh

$$+12 - 10I_0 - 5(3I_0) = 0$$

$$12 - 10I_0 - 15I_0 = 0$$


$$\frac{12}{25} = I_0$$

$$\begin{aligned} V_{th} &= 5(3I_0) \\ &= 5 \times 3 \times 12 \\ &= 36 \text{ V} \end{aligned}$$

$$V_{th} = 7.2 \text{ V}$$

For Δ Thevenin resistance w.r.t open terminal short voltage
current

For Thevenin resistance

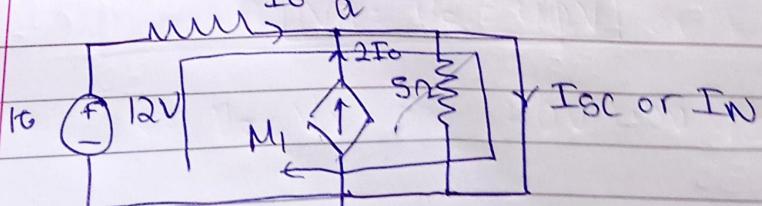

KCL at a

$$I_0 + 2I_0 = 3I_0 = I_{SC}$$

$$\therefore I_{SC} = 3I_0$$


KCL in M1

$$+12 - 10I_0 = 0$$


$$\frac{12}{10} = I_0$$

$$\therefore I_{SC} = 3I_0 = 3\left(\frac{12}{10}\right) = 3.6A$$

$$\therefore \text{Thevenin's resistance} = \frac{V_{TH}}{I_{SC}} = \frac{36}{\frac{3.6}{2}} = 22$$

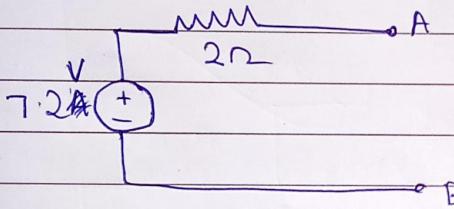 \therefore The Thevenin's equivalent is

Ans 11)

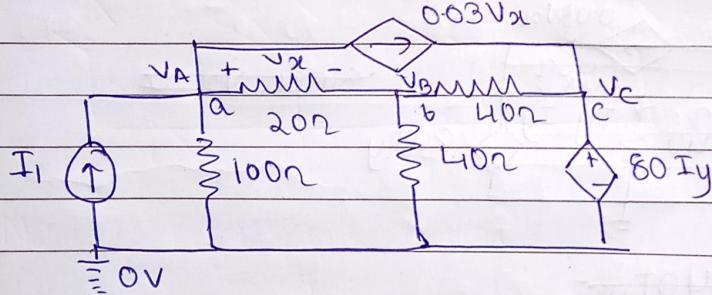

$$I_1 = 0.03V_x + V_A, V_B, V_x$$

Nodal analysis at a

$$I_1 = 0.03V_x + \frac{V_A}{100} + \frac{V_A - V_B}{20}$$

$$0.4 = 0.03V_x + 0.01V_A + 0.05V_x \quad (\text{where } V_A - V_B = V_x)$$

$$3V_x + 5V_x + V_A = 40$$

$$8V_x + V_A = 40 \quad \text{--- (1)}$$

Nodal analysis at -b

$$\frac{V_{2e}}{20} = I_y + \frac{V_B - V_c}{40} \quad \text{--- (2)}$$

Nodal analysis at c $V_c = 80I_y \quad \text{--- (3)}$

$$\therefore \frac{V_B}{40} = I_y \quad \text{--- (4)}$$

$$V_c = 2V_B \quad \text{--- (5)}$$

From (2) (5)

$$\frac{V_x}{20} = \frac{V_B}{40} + \frac{-V_B}{40}$$

$$\therefore \frac{V_x}{20} \sim 0$$


20

$$\therefore \boxed{V_x = 0}$$

From (1)

$$8(0) + V_A = 40$$

$$\therefore \boxed{V_A = 40}$$

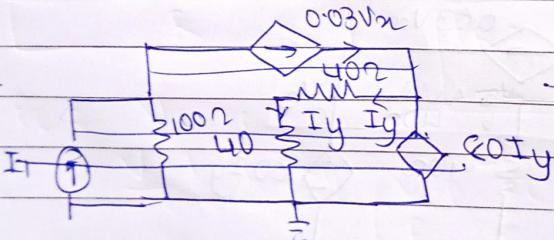

$$+40Iy + 40Iy =$$


$$\text{Since } V_A - V_B = V_{2e}$$

$$V_A - V_B = 0$$

$$\therefore \boxed{V_A = V_B = 40V}$$

$\therefore V_A, V_B, V_x \text{ are } 40V, 40V \text{ and } 0V$

Ans 12)

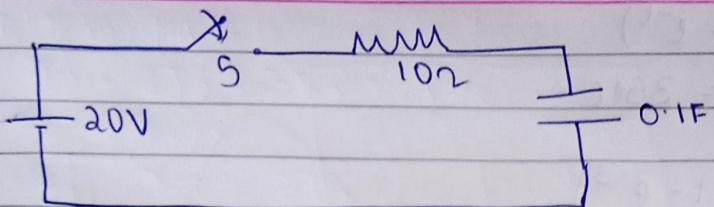

Ans 12) $i(t) = \frac{V}{R} e^{-\frac{t}{RC}}$ (Current as a Fⁿ of time)

$\therefore \tau = \text{Time constant} = RC = 10 \times 0.1 = 1 \text{ s}$

~~$i(t) = \frac{20}{10} e^{-\frac{t}{1}} = 2e^{-t}$~~

~~$i(0) = 2e^0 = 2 \text{ A at } t=0+ \text{ sec}$~~

At $t = 2\tau$

$$= 2(1 \text{ s})$$

$$= 2 \text{ s}$$

$$\therefore i(t) = 2e^{-t} =$$

$$\begin{aligned} \text{At } t = 2\tau & \quad i = 2e^{-2} \\ & = \frac{2}{e^2} \end{aligned}$$

$$i = 0.2706 \text{ A}$$

Ans 12) Voltage across capacitor

~~$V_C = V e^{-\frac{t}{RC}}$~~

$$\begin{aligned} V_C &= V \left(1 - e^{-\frac{t}{RC}}\right) \\ &= 20 \left(1 - e^{-\frac{t}{1}}\right) \\ &= 20(1 - e^{-t}) \end{aligned}$$

Voltage across resistor

$$\begin{aligned} V_R &= V e^{-\frac{t}{RC}} \\ &= 20 e^{-\frac{t}{1}} \\ &= 20 e^{-t} \end{aligned}$$

iv)

$$\text{Ans} \quad V_C = 20(1 - e^{-t})$$

$$\text{At } t = 3T = 3\pi \text{ sec}$$

$$\boxed{V_C = 20(1 - e^{-3})}$$

$$\boxed{V_C = 19.004 \text{ V}}$$

$$V_R = 20e^{-t}$$

$$\text{At } t = 3T = 3\pi \text{ sec}$$

$$V_R = \frac{20}{e^3} = 0.9957 \text{ V}$$

$$\boxed{V_R = 0.9957 \text{ V}}$$

$$\text{Ans} \quad P_R = V_R I_R R \quad (\text{if } R)$$

$$= \frac{V e^{-t}}{RC} \times R$$

$$P_R = V_R i_R$$

$$= V e^{-t} \frac{V}{R} e^{-\frac{t}{RC}}$$

$$\boxed{P_R = \frac{V^2}{R} e^{-\frac{2t}{RC}}}$$

For transistor

$$\boxed{P_R = \frac{400}{10} e^{-\frac{2t}{1}} = 40 e^{-2t}}$$

$$\text{ii) } P_C = V_C i_C$$

$$= V(1 - e^{-\frac{t}{RC}}) \left(\frac{V}{R} e^{-\frac{t}{RC}} \right)$$



$$P_C = \frac{V^2}{R} \left(e^{-\frac{t}{RC}} - e^{-\frac{2t}{RC}} \right)$$

$$P_C = \frac{400}{10} \left(e^{-\frac{t}{1}} - e^{-\frac{2t}{1}} \right) \quad RC = 1$$


$$\boxed{P_C = 40 (e^{-t} - e^{-2t})} \quad \text{For Power of capacitor}$$

20CSE1017

Pg 13

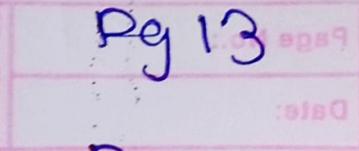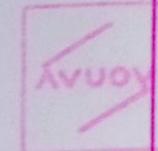

Ans vi)

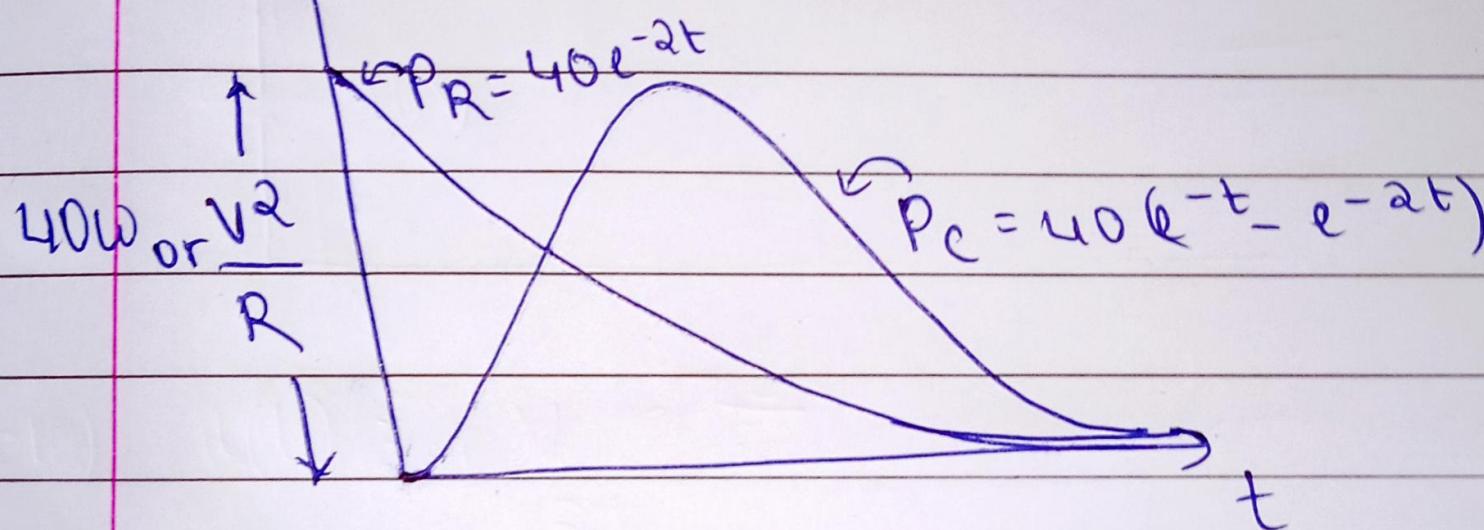

20CSE 1017
Pg 7

Page No.

Date:

