

## Chapter-4 Assignment

Due Date: 27<sup>th</sup> March 2021

Extended: 30<sup>th</sup> March 2021

### 1. Solve the below

- i.  $(658.825)_{10} = (\quad)_8$
- ii.  $(532.65)_{10} = (\quad)_{16} = (\quad)_2$
- iii.  $(5372.65)_{\text{8}} = (\quad)_{10} = (\quad)_2$
- iv.  $(9398.65)_{16} = (\quad)_8 = (\quad)_2$
- v.  $(11000110.010101)_2 = (\quad)_{10} = (\quad)_8 = (\quad)_{16}$
- vi.  $(ABCDE.F\cancel{C})_{16} = (\quad)_{10} = (\quad)_8$

### 2. Perform the below using 1s complement and 2s complement independently

- a.  $(56)_{10} - (34)_{10}$
- b.  $(85)_{10} - (105)_{10}$
- c.  $(65)_{10} - (155)_{10}$

### 3. Write the Graphical Symbol, Boolean Expression's function, Switch representation and Truth Table for the following Gates





- a. OR
- b. AND
- c. NOT
- d. NOR
- e. NAND
- f. Exclusive-OR
- g. Exclusive-NOR

### 4. Consider three inputs to a GATE and represent the following symbolically

- a. 3 input NOR Gate
- b. 3 input NAND Gate
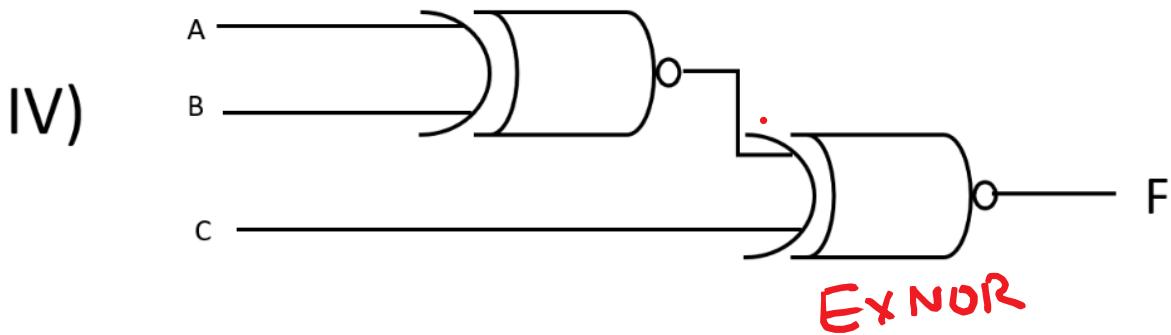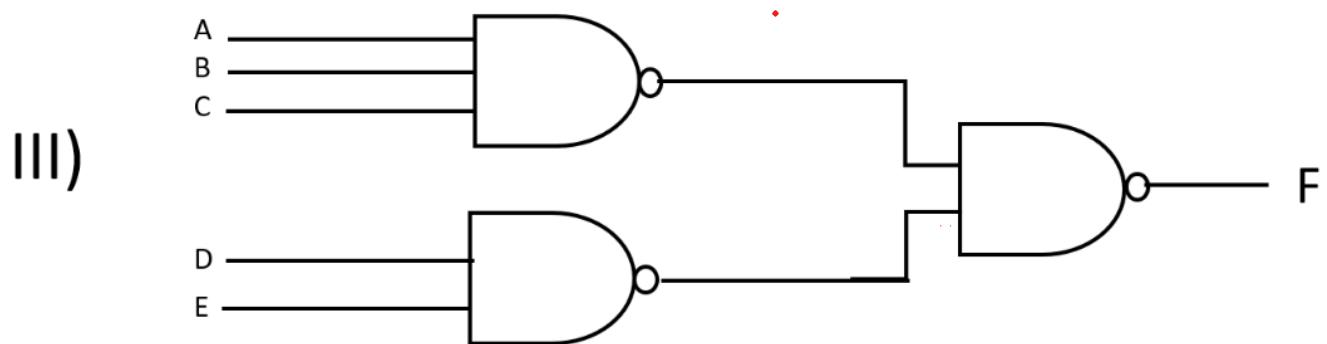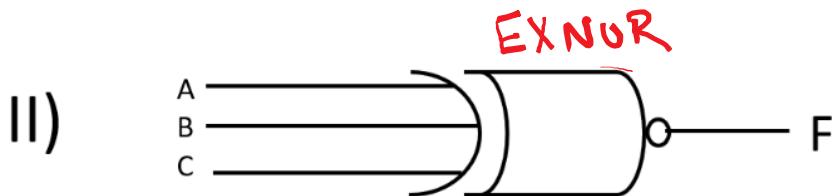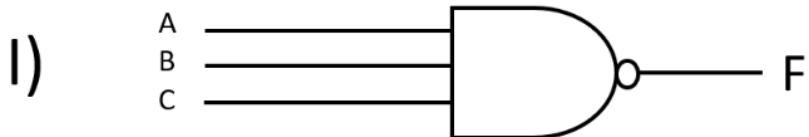
## 5. For the following Gate inter Connections

- Write the output Boolean expression (i.e., F)
- Truth Table of 'F'



## 6. Simplify the following Boolean Expressions to a minimum number of literals (ie., variables)

a.  $AB + A + AB$  (Ans: A)

b.  $\overline{A\bar{B}} + ABC + A(B + A\bar{B})$  (Ans: 0)

c.  $\overline{ABC} + \overline{ABC} + \overline{BA} = 1$  (Ans: ~~AB+BC~~)

d.  $\overline{AB} + \overline{ABC} + A(B + A\bar{B})$  (Ans: 0)

e.  $\overline{A} + AB + A\bar{C} + \overline{ABC} \rightarrow 1$  (Ans: ~~A+B+C~~)

f.  $(A+B)(A+\bar{B})$  (Ans: A)

g.  $\overline{AB}(\overline{D} + \overline{CD}) + B(A + \overline{AC}D)$  (Ans: B)

h.  $(\overline{A}+C)(\overline{A}++\overline{C})(A + B + \overline{CD})$  (Ans:  $\overline{A}(B+\overline{C}D)$ )

## 7. Realize the below Boolean expressions using logic gates

a.  $F = AB + C\bar{D} + \bar{B}C$

b.  $F = (A+B)(\bar{C} + \bar{B})(\bar{D} + D + E)$

## 8. Given the following Boolean Function

$$F = \overline{ABC} + \overline{ABC} + \overline{D}AB + \overline{D}\bar{A}B + DAB$$

- Obtain the truth table for the given function 'F'
- Draw the logic gate diagram using Boolean expression
- Simplify the function to a minimum number of literals using Boolean algebra  
(Ans:  $\bar{B}C + B(D + A)$ )
- Obtain the truth table using the simplified function obtained from 8(c)

PPT

## 9. Write in brief about the following Memory Elements:

SRAM, DRAM, ROM, PROM, EPROM, EEPROM.

Reference Book for Digital Electronics: 'Digital Design' by Morris Mano

\*\*\*\*\*